

ECGR 3183 Project

Instruction Set

Each of our instructions is encoded in a 32 bit word. The opcode portion of the instruction maps to a 5 bit value at the most significant bits. Following that the destination register and the two source register addresses follow taking up 4 bits each. The first source register specified corresponds to the ‘top’ register in the design. This register will always be sent to the ALU, and is used for instructions that only require one input or who’s values need to be passed through the ALU unmodified. The second register can be used as a second value for the ALU, but also can be redirected into the data memory for storage. For branching instructions the label will be encoded into the final 10 bits of the instruction, allowing for a branch destination to be any available memory address. That leaves 5 unused bits between the final source register and the beginning of the branch label for a total of 32 bits.

Our instruction set is as follows:

Instruction	Op Code	Syntax	Description	Condition Codes
Set	10000	SET Rd #Value	Sets a specified value into a register	None
Load	10001	LOAD Rd Ri	Takes a value from memory at address in register Ri and stores it in register Rd	None


Store	10010	STORE Rd Ri	Stores a value located in register Ri into memory at address stored in Rd	None
Move	10011	MOVE Rd Ri	Moves the value in register Ri into register Rd	None
Add*	00000	ADD Rd Ri Rj	Adds the values in registers Ri and Rj together and stores the result in Rd	Z N
Subtract*	00001	SUB Rd Ri Rj	Subtracts the values in register Ri from the one in Rj and stores the result in Rd	Z N
Negate*	00010	NEG Rd Ri	Multiplies the value in Ri by -1 and stores the result in Rd	Z N
Multiply	00011	MUL Rd Ri Rj	Multiplies the values in Ri and Rj together and stores the result in Rd	Z N
Divide	00100	DIV Rd Ri Rj	Divides the value in Ri by the one in Rj and stores the result in Rd	Z N E
Floor*	00101	FLOOR Rd Ri	Rounds the value in Ri down to the nearest integer and stores the result in Rd	Z N
Ceiling*	00110	CEIL Rd Ri	Rounds the value in Ri up to the nearest integer and stores the result in Rd	Z N
Round*	00111	ROUND Rd Ri	Rounds the value in Ri to the nearest even	Z N

			integer and stores the result in Rd	
Absolute*	01000	ABS Rd Ri	Takes the absolute value of the value in Ri and stores the result in Rd	Z N
Minimum*	01001	MIN Rd Ri Rj	Stores the smaller value in Ri and Rj into Rd	Z N
Maximum*	01010	MAX Rd Ri Rj	Stores the larger of the values in Ri and Rj into Rd	Z N
Power	01011	POW Rd Ri #Value	Raises the value in register Ri to the immediate value and stores the result in Rd	Z N
Exponent	01100	EXP Rd Ri	Calculates the value of e raised to the power in Ri and stores the result in Rd	Z N
Square Root	01101	SQRT Rd Ri	Takes the square root of the value in Ri and stores the result in Rd	Z N
Unconditional Branch	11010	UB LABEL	Moves the PC to the line marked with the specified label	None
Negative Branch	11000	BN Ri LABEL	Moves the PC to the line marked with the specified label if the value in Ri is negative	N
Zero Branch	11001	BZ Ri LABEL	Moves the PC to the line marked with the specified label if the value in Ri is zero	Z
No-op	11111	PASS	Does nothing for one cycle	None

Halt	10101	HALT	Stops execution of the program	None
------	-------	------	--------------------------------	------

* Implemented at the bit level

Single Cycle

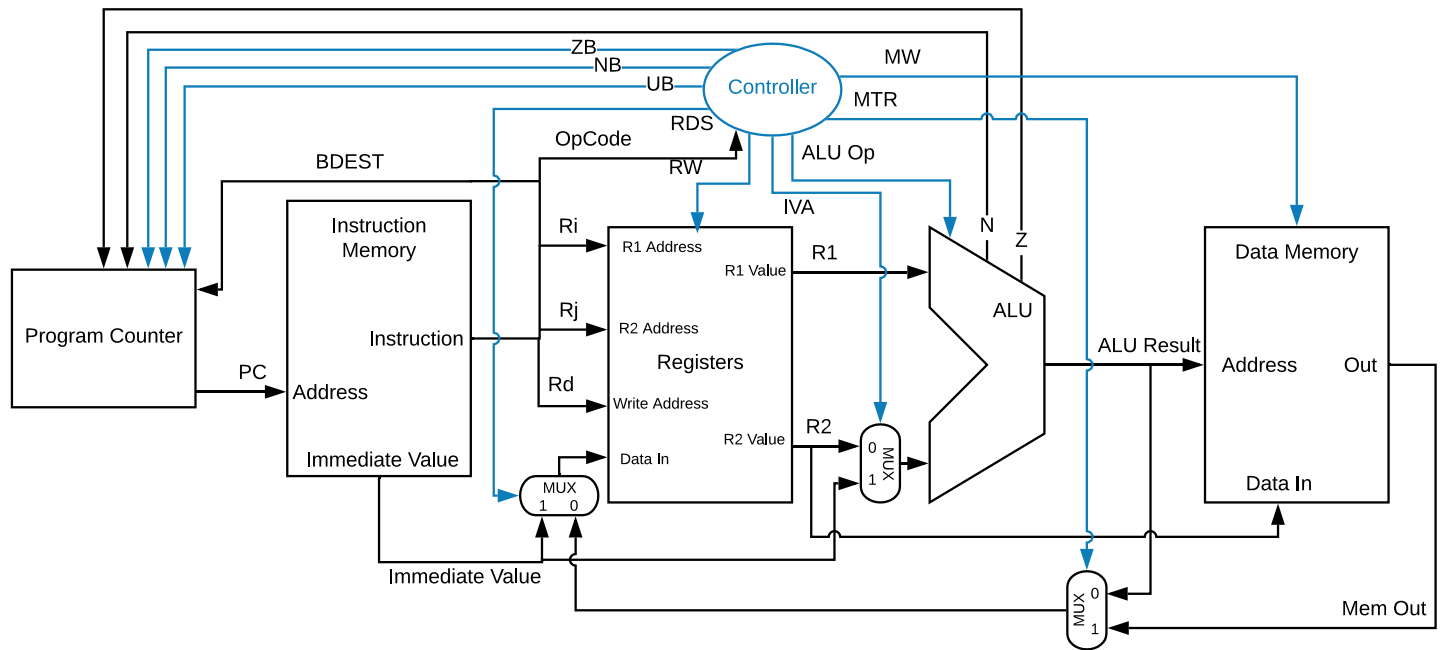

Data Path

Controller Signals:

- UB – Unconditional Branch {1: Branch unconditionally, 0: Don't do that}
- ZB – Branch on Zero {1: Branch if zero flag from ALU is set, 0: Don't do that}
- NB – Branch on Negative {1: Branch if negative flag from ALU is set, 0: Don't do that}
- ALUC – ALU Control Signal {4 bit signal for ALU ops}
- RW – Register Write {1: Write data to Rw address, 0: Don't do that}
- MW – Memory Write {1: Write data to memory address, 0: Read data from memory address}
- MTR – Memory to Register {0: Send ALU result to register, 1: Send memory result to register}
- RDS – Register Data Source {1: Immediate Value, 0: Memory/ALU}

- IVA – Immediate Value to ALU {1: Use immediate value, 0: use register output}

Controller Signals

Op Code	ALUC	UB	ZB	NB	RW	MW	MTR	RDS	IVA
SET	1111*	0	0	0	1	0	X	1	0
LOAD	1111*	0	0	0	1	0	1	0	0
STORE	1111*	0	0	0	0	1	X	0	0
MOVE	1111*	0	0	0	1	0	0	0	0
ADD	0000	0	0	0	1	0	0	0	0
SUB	0001	0	0	0	1	0	0	0	0
NEG	0010	0	0	0	1	0	0	0	0
MUL	0011	0	0	0	1	0	0	0	0
DIV	0100	0	0	0	1	0	0	0	0
FLOOR	0101	0	0	0	1	0	0	0	0
CEIL	0110	0	0	0	1	0	0	0	0
ROUND	0111	0	0	0	1	0	0	0	0
ABS	1000	0	0	0	1	0	0	0	0
MIN	1001	0	0	0	1	0	0	0	0
MAX	1010	0	0	0	1	0	0	0	0
POW	1011	0	0	0	1	0	0	0	1
EXP	1100	0	0	0	1	0	0	0	0
SQRT	1101	0	0	0	1	0	0	0	0
UB	1111*	1	0	0	0	0	X	0	0
ZB	1111*	0	1	0	0	0	X	0	0

NB	1111*	0	0	1	0	0	X	0	0
NOP	1111*	0	0	0	0	0	X	0	0
HALT	1111*	1	0	0	0	0	X	0	0

* 1111 is PASS op to ALU. It will pass whatever is on its first input through to its output.

Doubles as no-op/don't care command as output value can be ignored when not needed

Notes:

- The PC receives the various control signals it needs to compute its next value. Since immediate values are provided by the instruction memory for all instructions, the PC jumps by 2 addresses by default.
- HALT operation is implemented as an unconditional branch to the same address.
Once the HALT command is reached, the PC will remain locked to that memory address. (Probably a bad idea)
- MTR in the chart above are set to don't care (X) when overriding signals around the register negate their impact. For example, if the register write signal is off (no data is being written to the register), the value that reaches the register through the muxes doesn't matter.

Memory Elements

Instruction Memory, Register File, Data Memory & Stage Registers

Instruction Memory:

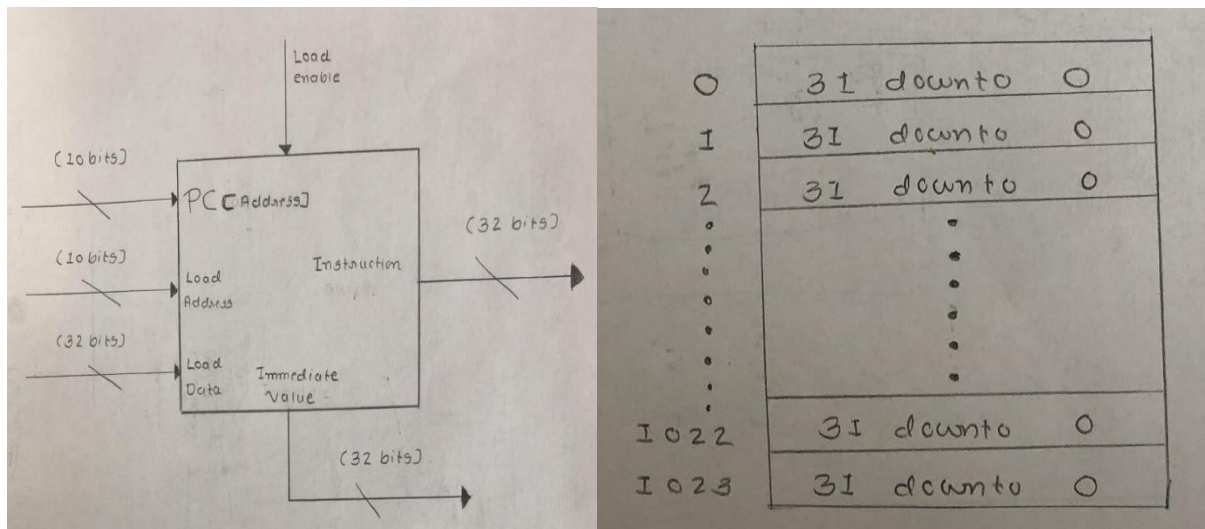


Figure 1: Black Box Diagram of Instruction Memory

Above image 1, shows the diagram of the instruction memory. Instruction memory is designed to have a capacity of storing 1024 words maximum at once (4096 bytes). As shown in figure, it has four input ports and two output ports. For the Program Counter and load address ports 10 bits signal ports are used to index the particular word of data from 1024 different word(1 word = 32 bits) values. Load Data port is used to transfer the data to instruction memory

when load enable signal is high (once while loading the program). For output, two ports of 32 bits are assigned. Instruction output signal is used to omit out the pointed instruction data by PC. While the Immediate value signal carry outs the immediate value stored on instruction memory.

For the stimulation of the instruction memory, 1024 arrays each of 32 bits were created using the VHDL code. Instruction memory is programmed to omit out one word of instruction data and reading new PC value on every rising edge of clock. For loading the new data to instruction memory, load data port is used to transfer the new data and load address is used for pointing the load location for new data. While load enable port is used to activate the load data and load address ports. Finally, the immediate values according to ISA uses 32 bits (entire block of word) so, the instruction consisting of immediate values omits out the entire block of word data followed by the one indexed by PC (PC+1) indexed value of particular instruction.

Register File:

 


Figure 2: Black Box Diagram of Register File

Above image 2, shows the diagram of the register file. Register file is designed for the processor consist of the sixteen different registers each of 32 bits. As demonstrated in diagram, it has five input ports and two output ports. 'R1 Address' and 'R2 Address' ports each with four-bit bus signal are used to point the two source registers from the register file similarly, 'Rd Address' port is used to point the destination register for the particular instruction. 'Data In' port with 32-bit bus signal is used for transferring(writing) the data to the destination register, when 'RW' signal is high. For output 'R1 value' and 'R2 value' ports each assigned with 32 bits bus signal for passing the source register data to ALU for execution stage.

For stimulating the register file, 16 arrays each of 32 bits were created using the VHDL code. Register memory is programmed to output data at output ports on every rising edge of the clock cycle and read new input values pointing to the other new two source registers. For writing the data to destination register on the register file, 'RW' signal is activated then, 'Rd Address' port is used to point the destination register on the file and data is written through the 'Data In' port.

 
Data Memory:**Figure 3: Black Box Diagram of Data Memory**

Image 3 shows the diagram of the data memory. Data memory is designed to have capacity of storing 1024 words maximum at once (4096 bytes). As shown in the diagram, it has three input ports and one output port. 'Address' port is assigned the signal of 32 bits bus for indexing the particular word in data memory. 'Data In' port is used to transfer/write the data in the data memory when 'MW' signal is high. For the output 'Out' port is used, it also has 32-bit bus signal assigned to it. Output data then is written to destination register.

For stimulation of the data memory, 1024 arrays each of 32 bits were created using the VHDL coding. Data memory is programmed to omit out one word (1 word = 32 bits) of data and

read new 'Address' on every rising edge of clock cycle. For storing the new data in data memory 'Data In' port is used for writing the new data and 'Address' port is used to point location in memory. 'MW' signal is used to activate the both of the other input ports. At last, data omitted by 'Out' port is send to the 'Data In' port of the register file. The only issue faced while stimulating the data memory was that the 'Address' value calculated by the ALU was in format of floating-point numbers, so it became hurdle for indexing the location in memory. To fix that problem, function that converts the floating-point number to integer format was utilized.

Stage Registers:

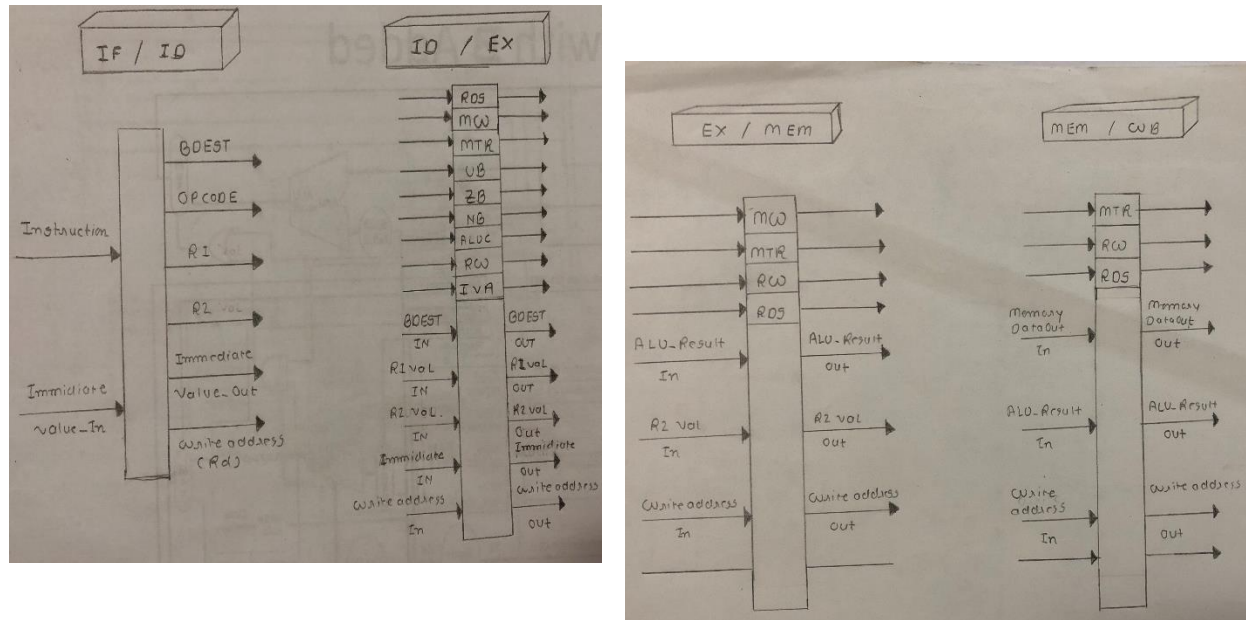


Figure 4: Black Box Diagram of four Stage Registers

As shown in figure 4, four stage registers are used while applying the pipeline on the processor. Each stage in processor pass its output signals along with the control signals to this stage registers and then stage registers pass those signals to next stage as per needed (by detecting hazards). For stimulation of these registers VHDL code was used. Basically, registers were designed to take the input in form of signal on rising edge of clock of clock, and omitted the signals for the rest. Below is the description of each stage register in brief:

IF/ID: This stage register receives the inputs from fetch stage components like instruction memory and passes output to decode stage component such as register file.

ID/EX: This stage register receives the inputs from decode stage components like register file and passes output to execution stage component such as ALU.

EX/MEM: This stage register receives the inputs from execution stage components like ALU and passes output to memory stage component such as data memory.

MEM/WB: This stage register receives the inputs from memory stage components like data memory and passes output back to destination register in register file.

PC

The program counter keeps track of the program's execution. It receives various control signals from the controller and ALU to determine branches. Since our instruction memory outputs both the instruction and any potential immediate values, the default increment for the value in the PC each cycle is two. On the single cycle design this is not necessary, but it avoids a lot of potential control hazards in the pipelined version.

ALU


Overall the ALU acts as a large multiplexer that takes two 32 bit inputs and performs different arithmetic operations on them based on the control signal it receives. After the result is computed, it also sends out a zero and negative flag for the PC to use to determine whether or not to branch.

The add function was easily one of the most harrowing tasks that our group encountered. One of the biggest issues with designing the addition function was handling the special cases of infinity and denormalized values. It also required a fair number of auxiliary functions such as shifting, two's complementing, and regular unsigned addition/subtraction to be designed to complete the task.


Pipeline

Waveforms:

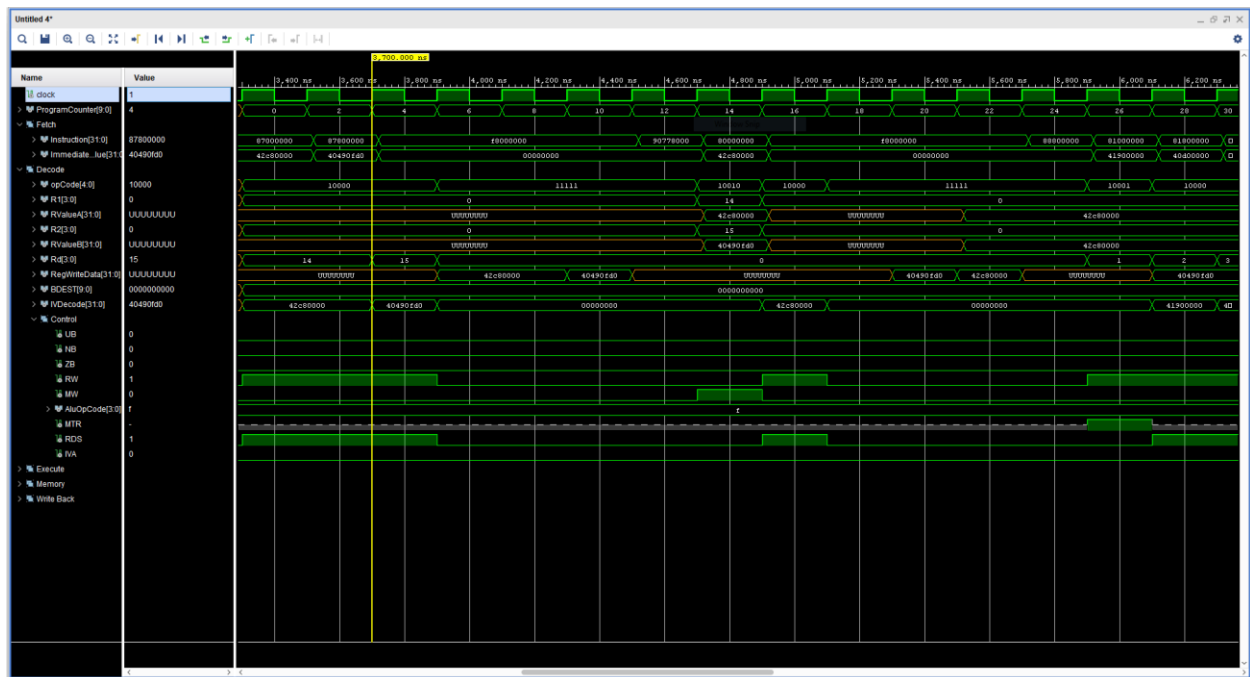
Fetch/Decode: Shows the various signals from the fetch and decode stages of the pipeline grouped together



 
Execute/Memory: Shows the various signals from the execute and memory stages of the pipeline grouped together



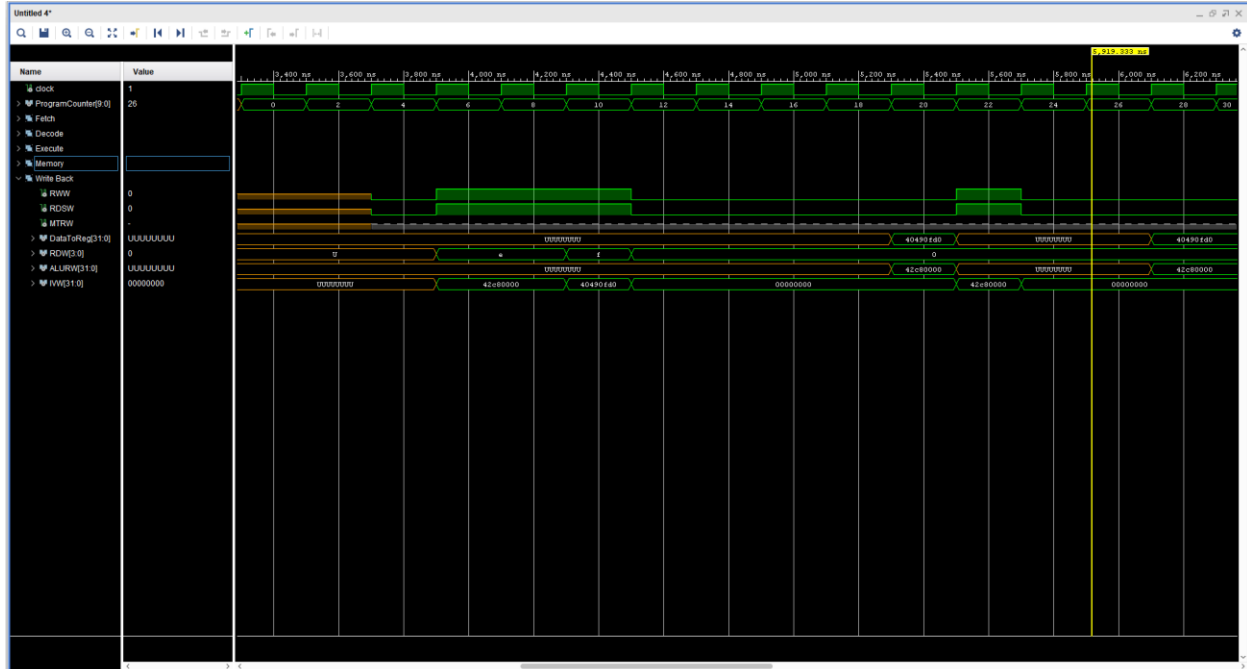Writeback: Shows the various signals from the write back stage of the pipeline grouped together



Pipelined Architecture

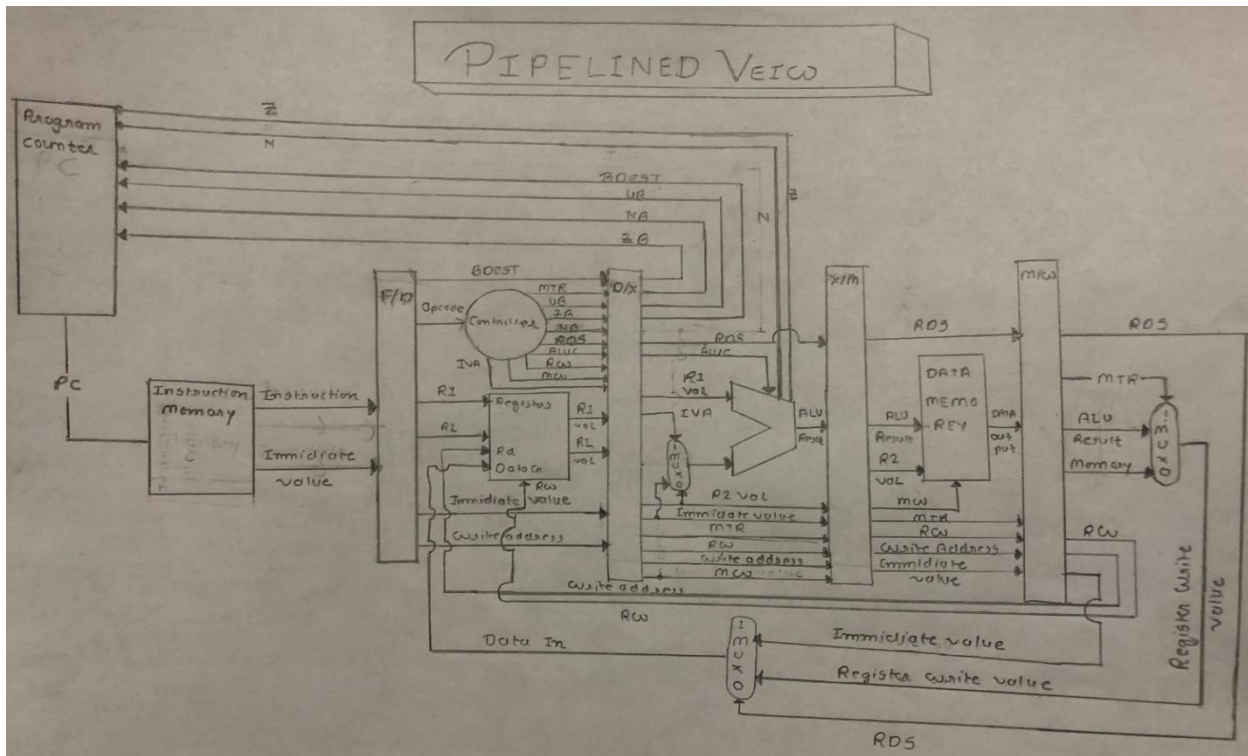

Note: The pipelined design was completed after the demo and now functions properly. It does not have hazard detection or forwarding so dependent instructions must have noops inserted between them to give the processor time to update the values required in the registers before they are used. (There wasn't enough time to write more about the pipeline).